

# Assignment 1

Krunal Badlani (IS21MTECH14008)

14 January 2022

## 1 Question

Draw the Logic Circuit of the following Boolean Expression :  
 $(U' + V).(V' + W')$

## 2 Answer

The circuit obtained would look like this:

